

Date: December-10-2024

Tuesday, December 10, 2024 8:16 PM

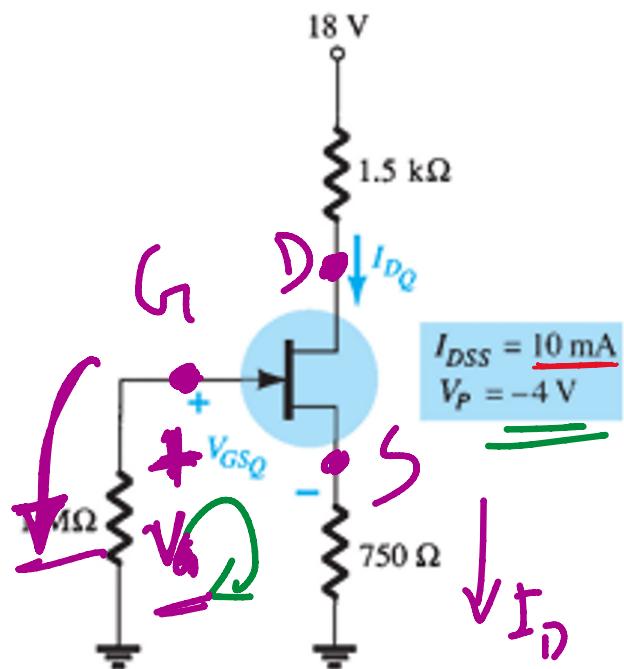


FIG. 7.80

Problems 6, 7, and 38.

$$I_D R_S + V_{GS} + I_D R_S = 0$$

$$\Rightarrow V_{GS} = -750 I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$= 10 \times 10^{-3} \left(1 - \frac{750 I_D}{4}\right)^2$$

init value	$I_D$	$V_{GS}$
0	2.61 mA	-1.96 ✓
10m	0.011 A	-8.18 ←

$$I_D = 2.61 \text{ mA} \quad \boxed{\text{Ans}}$$

$$V_{GS} = -1.96 \text{ V} \quad \boxed{\text{Ans}}$$

$$V_{DS} = V_{DD} - I_D R_D - \Sigma R_S$$

$$= 18 - - - -$$

$$= 12.13 \text{ V} \quad \boxed{\text{AM}}$$

$$V_D = V_{DD} - I_D R_D$$

$$= 14.085 \text{ V} \quad \boxed{\text{AM}}$$

$$V_h = I_G R_h = 0 \text{ V} \quad \boxed{\text{AM}}$$

$$V_S = \Sigma R_S = 1.958 \text{ V} \quad \boxed{\text{AM}}$$


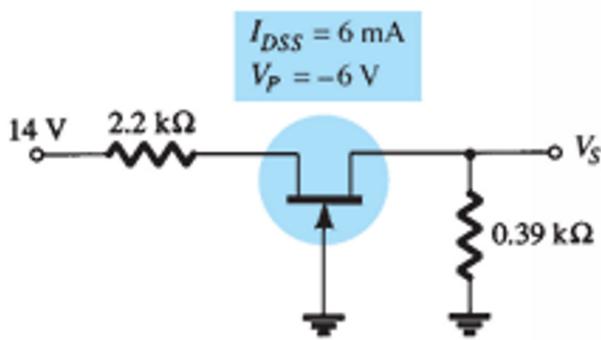


FIG. 7.84  
Problem II.

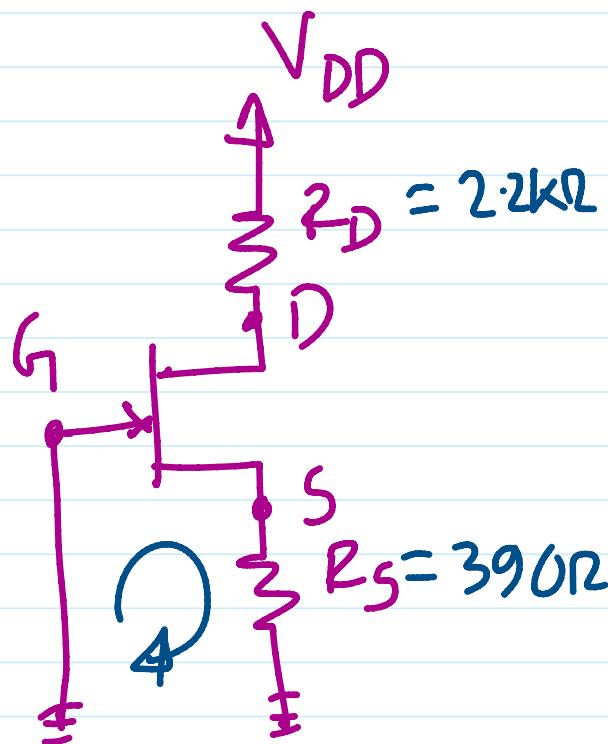

$$I_G R_G + V_{GS} + I_D R_S = 0$$

$$\Rightarrow V_{GS} = -390 I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$= 6 \times 10^{-3} \left(1 - \frac{390 I_D}{6}\right)^2$$

0: I\_D = 3.55 \text{ mA} \rightarrow V\_{GS} = -1.39 \text{ V}

$$V_s = I_D R_S =$$

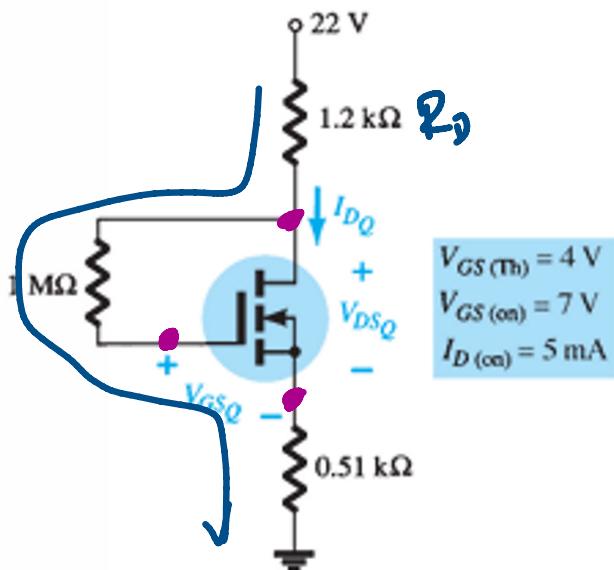


FIG. 7.94  
Problem 22.

$$22 = I_D R_D + V_{hs} + I_D R_S$$

$$\Rightarrow V_{hs} = 22 - I_D (R_D + R_S)$$

$$= 22 - I_D \times 1710$$

$$I_D = K (V_{hs} - V_{Th})^2$$

$$K = \frac{I_{DS(\text{on})}}{(V_{DS(\text{on})} - V_{Th})^2} = \frac{5 \times 10^{-3}}{(7 - 4)^2}$$

$$= \frac{5}{9} \text{ mA/V}^2$$

$$I_D = \frac{5}{9} \times 10^{-3} \left( 22 - 1710 I_D - 4 \right)^2$$

$$I_D = \frac{g}{2} \cdot I_V \cdot \left( \frac{V_{DS}}{2} - V_{GS} \right)^2$$

$$= \frac{5}{2} \times 10^{-3} (18 - 1710 I_D)^2$$

O:  $I_D = 8.27 \text{ mA}$   $\Rightarrow V_{GS} = 7.86 \text{ V}$

$$I_D = 8.27 \text{ mA}$$

$\Delta V$


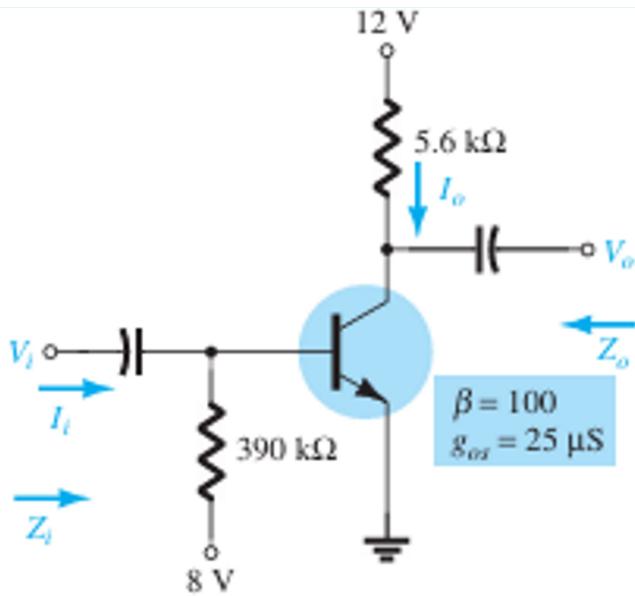


FIG. 5.153  
Problem 13.

$$\gamma_o = \frac{1}{g_B} = 40 \text{ k}\Omega$$

12V  
5.6 kΩ

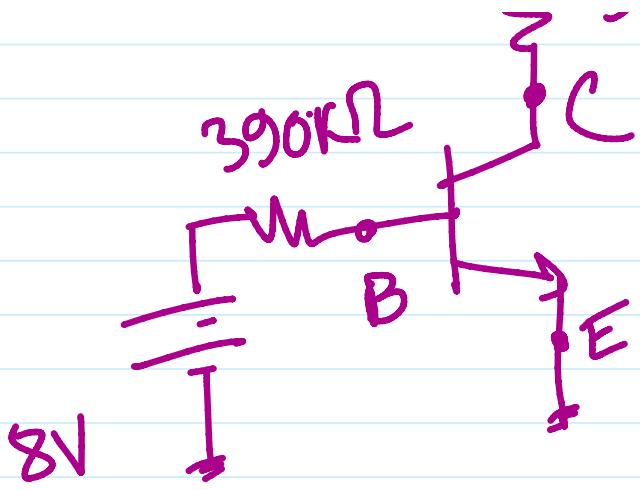

$$I_B = \frac{8 - 0.7}{390 \times 10^3}$$

$$= 18.72 \text{ mA}$$

$$I_E = (1 + \beta) I_B = 1.89 \text{ mA}$$

$$\gamma_e = \frac{V_T}{I_E} = \frac{26}{1.89} = 13.76 \Omega$$


$$Z_i = R_B \parallel \beta \gamma_e = 390 \times 10^3 \parallel 100 \times 13.76$$

$$= 1371.16 \Omega \quad \boxed{\text{Ans}}$$

$$Z_o = \gamma_o \parallel R_C = 40 \times 10^3 \parallel 5.6 \times 10^3$$

$$= 4912.28 \Omega \quad \boxed{\text{Ans}}$$

$$A_U = -\frac{\gamma_0 \parallel R_C}{\gamma_e} = -357 \quad \boxed{Am}$$

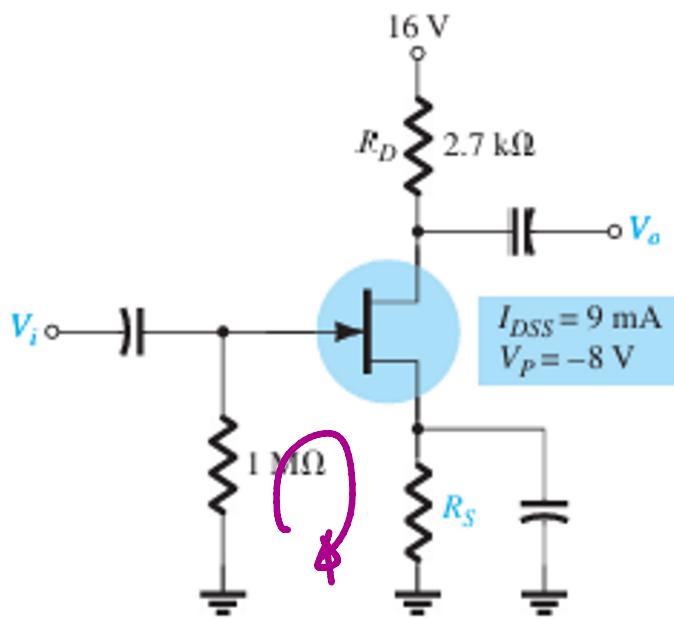

**FIG. 8.74**  
Problem 23.

$$g_m = \frac{dI_D}{dV_{DS}}$$

$$\therefore g_m = \frac{2I_{DSS}}{|V_P|} \left( 1 - \frac{V_{DS}}{V_P} \right)$$

$$\therefore g_m = \frac{2 \times 9 \times 10^{-3}}{8} \left( 1 + \frac{V_{DS}}{8} \right)$$

$$\Rightarrow -2 = -g_m \times 2.7 \times 10^3$$

$$\therefore g_m = 74074 \times 10^{-6} \quad \text{A/V}$$

$$\Rightarrow 740.74 \times 10^{-6} = \frac{2 \times 9 \times 10}{8} \left( 1 + \frac{-5.37}{8} \right)$$

$$\Rightarrow V_{ns} = -5.37 \text{ V}$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{ns}}{V_P} \right)^2$$


$$= 0 \left( 1 - \frac{5.37}{8} \right)^2$$

$$= 0.973 \text{ mA}$$


$\nearrow I_n R_o + V_{ns} + I_D R_S = 0$

$$\Rightarrow R_S = - \frac{V_{ns}}{I_D} = \frac{5.37}{0.973 \times 10^{-3}}$$

$$= 5519.01 \text{ } \boxed{\Omega}$$

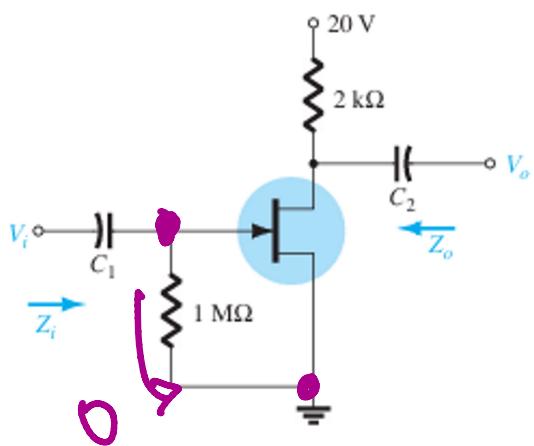

**FIG. 8.75**  
Self-bias configuration for Problems 24 and 60.

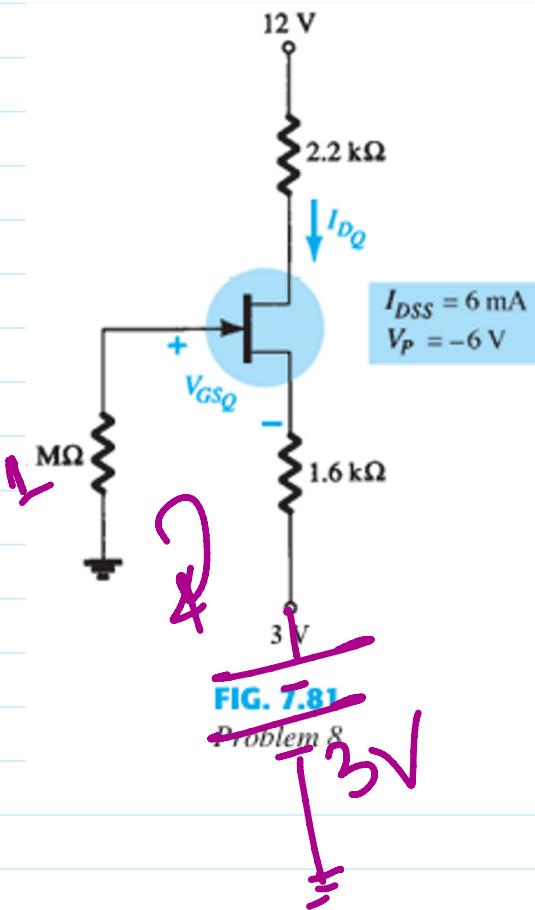

**FIG. 7.81**

Problem 8

$$I_{DRS} + V_{DSQ} + I_{DRY} + 3 = 0$$

$$\therefore V_{DS} = -3 - I_{DRY}$$

$$I_D =$$