

Department of ECE, NSU

EEE111/ETE111 Assignment

Due Date: 07-Dec-2024

Full marks: 05

Name:

Std No:

Q. For the circuit shown, plot the input impedance Z_i and the voltage gain A_v with varying β , assuming $r_o = \infty$. A sample plot is shown below. You can use Python or any other language of your choice.

